



Lodz University of Technology  
Institute of Physics

Laboratory of electronics

Exercise E13IFE

Power supply

## **Table of contents:**

1. Purpose of the exercise .....	3
2. Hazards .....	3
3. Introduction .....	3
4. Available equipment .....	5
4.1. Multimeters .....	5
4.2. Oscilloscope .....	6
4.3. Experimental modules of the power supply .....	6
5. Experimental procedure .....	9
5.1. Basic version .....	9
5.2. Extended version .....	10
6. Report elaboration .....	11
7. References .....	11
7.1. Basic reference materials .....	11
7.2. Other reference materials .....	11
8. Appendixes .....	12
A1. Table of passive electronic components .....	12

Before you start to perform an experiment you are obliged to have mastered the following theoretical subjects:

1. Semiconductor rectifier diodes. [1], [2].
2. Half-wave rectifier. [1].
3. Full-wave rectifier. [1].

## 1. Purpose of the exercise

The comprehension and measurement of the semiconductor rectifiers is the purpose of this experiment. The half-wave and full-wave silicon diode rectifiers with and without low-pass output filters are investigated.

## 2. Hazards

Type	Absence	Low	Medium	High
electrical radiation hazards		+		
optical radiation hazards	+			
mechanical hazards (including acoustic hazards, noise)	+			
electromagnetic radiation hazards (invisible)	+			
biological hazards	+			
ionizing radiation hazards	+			
chemical hazards	+			
thermal hazards (including explosion and fire)	+			

The cables with banana plugs are designed exclusively for use in low-voltage circuits - do not connect them to the mains supply 230 V.

## 3. Introduction

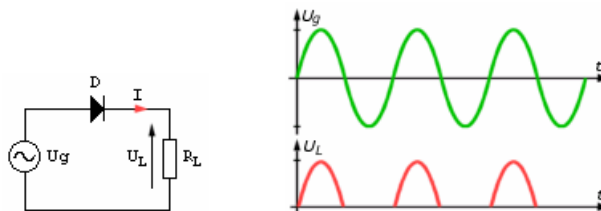


Fig.1. Schematic diagram of half-wave rectifier circuit and oscillograms of input  $U_g$  and output  $U_L$  voltage signal [4].

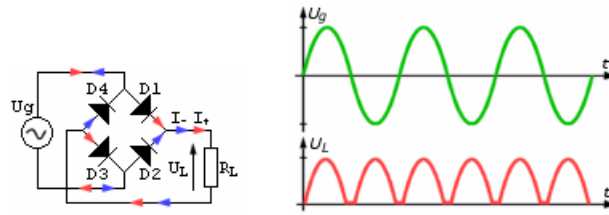


Fig.2. Schematic diagram of full-wave rectifier circuit and oscillograms of input  $U_g$  and output  $U_L$  voltage signal [4].

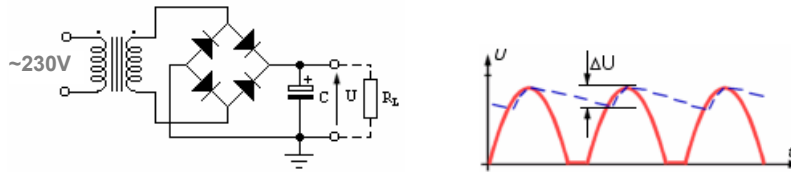


Fig.3. Schematic diagram of full-wave rectifier circuit with simple capacitor filter and oscillogram of output  $U$  voltage signal [4].

In order to ensure low AC ripple voltage at the load  $R_L$  the following condition should be satisfied

$$R_L \cdot C \gg 1/f. \quad (1)$$

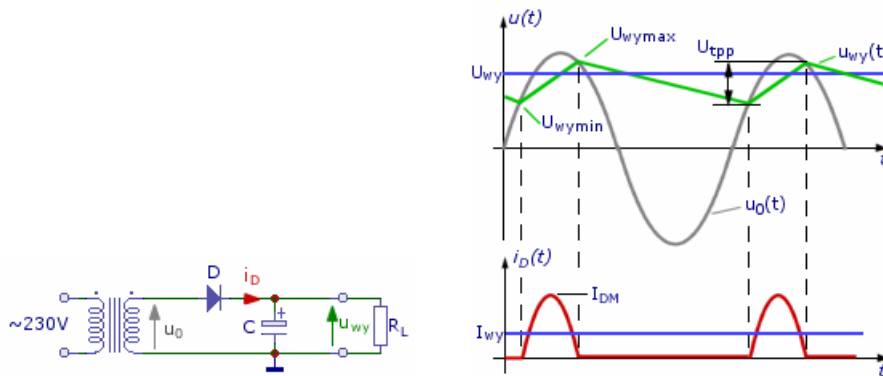


Fig.4. Schematic diagram of half-wave rectifier circuit with simple capacitor filter and oscillograms of output signals of voltage and diode current [4].

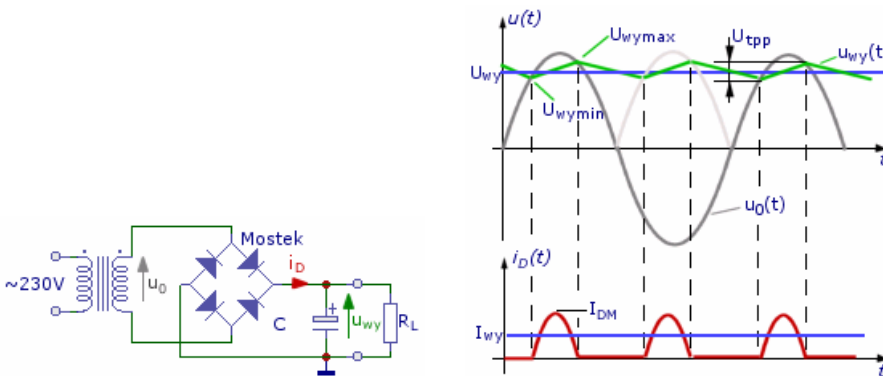


Fig.5. Schematic diagram of full-wave rectifier circuit with simple capacitor filter and oscillograms of output signals of voltage and diode current [4].

The ripple peak-to-peak voltage at the output of simple capacitor filter is given by

$$\text{- for half-wave rectifier: } U_{\text{tpp}} \approx \frac{I_{\text{wy}}}{C \cdot f} \quad , \quad (2)$$

$$\text{- for full-wave rectifier: } U_{\text{tpp}} \approx \frac{I_{\text{wy}}}{2 \cdot C \cdot f} \quad , \quad (3)$$

where  $f = 50\text{Hz}$  is the frequency of power line and  $I_{\text{wy}}$  is the DC component of the output current.

Assuming that the ripple signal at the output of full-wave rectifier with a smoothing capacitor has a triangular shape (see Fig. 5, the green curve) the root mean square (rms) value of the ripple voltage can be found as

$$U_{\text{sk}} = \frac{U_{\text{tpp}}}{2\sqrt{3}} \quad . \quad (4)$$

Experimental values of ripple factors may be defined employing rms value  $U_{\text{sk}}$  as well as peak-to-peak value  $U_{\text{tpp}}$  of ripple voltage:

$$k_t = \frac{U_{\text{sk}}}{U_{\text{wy}}} \quad , \quad (5)$$

$$M_t = \frac{U_{\text{tpp}}}{U_{\text{wy}}} \quad , \quad (6)$$

For the circuit shown in Fig. 5 theoretical values of ripple factors are:

$$k_t = \frac{1}{4\sqrt{3} \cdot f \cdot C \cdot R_L} \quad , \quad (7)$$

$$M_t = \frac{1}{2 \cdot f \cdot C \cdot R_L} \quad . \quad (8)$$

## 4. Available equipment

### 4.1. Multimeters

The voltages and currents in the experimental module will be measured using digital multimeters. The following models may be used: Metex, model M-3800 or M-4650, Protek 506, UNI-T UT804, or KEMOT KT890 [3].

## 4.2. Oscilloscope

The waveforms on input and output of the experimental modules are observed on a dual channel oscilloscope SDS1052DL [3].

## 4.3. Experimental modules of the power supply

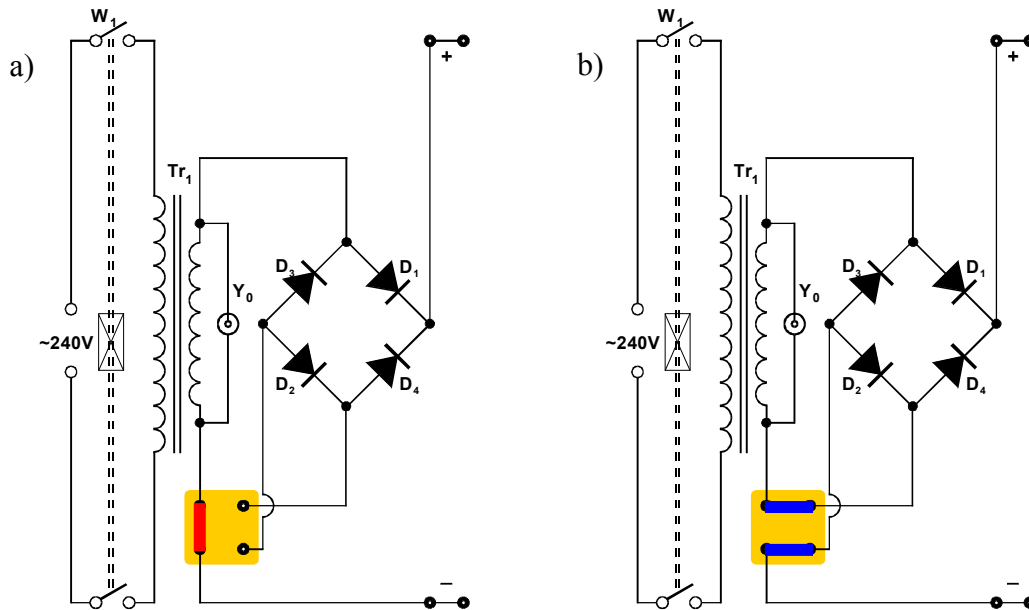


Fig. 6. Configuration mode of rectifier to work as (a) half-wave (red color jumper) or (b) full-wave (blue color jumpers).

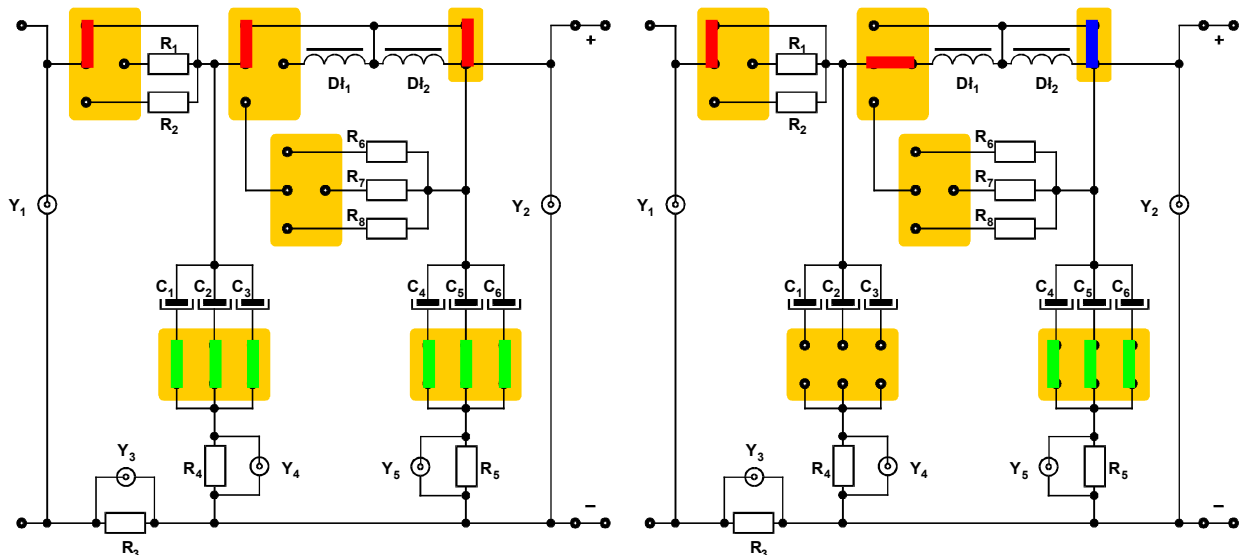


Fig. 7a. Simple capacitor filter. Red color jumpers are fixed. Green color jumpers are used to change the capacitance of filter.

Fig. 7b. LC filter of  $\Gamma$  type. Red color jumpers are fixed. Green color jumpers are used to change the capacitance of filter. Blue color jumper is used to short/unshort the  $DI_2$  choking coil (to decrease/increase inductance).

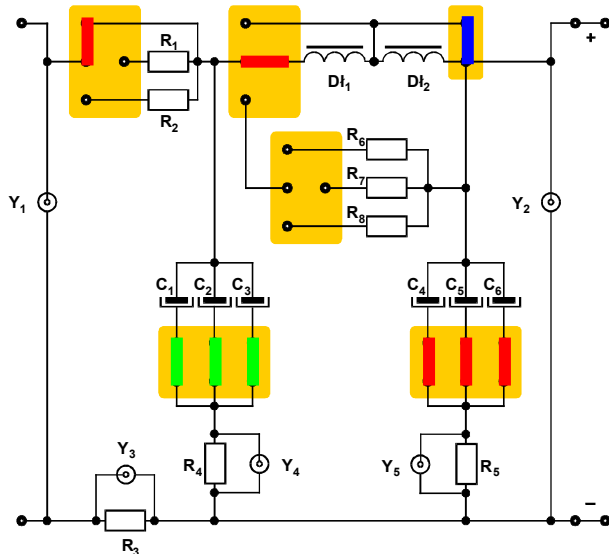


Fig. 7c. LC filter of II type. Red color jumpers are fixed. Green color jumpers are used to change the capacitance of filter. Blue color jumper is used to short/unshort the  $DI_2$  choking coil (to decrease/increase inductance).

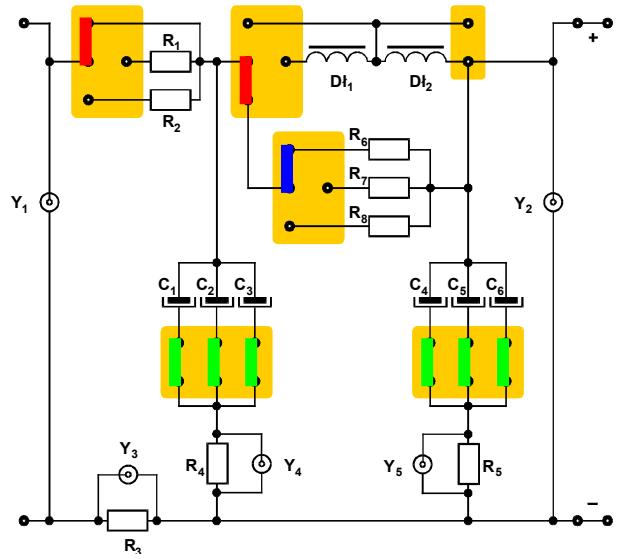


Fig. 7d. RC filter of II type. Red color jumpers are fixed. Green color jumpers are used to change the capacitance of filter. Blue color jumper is used to select one of three different resistances.

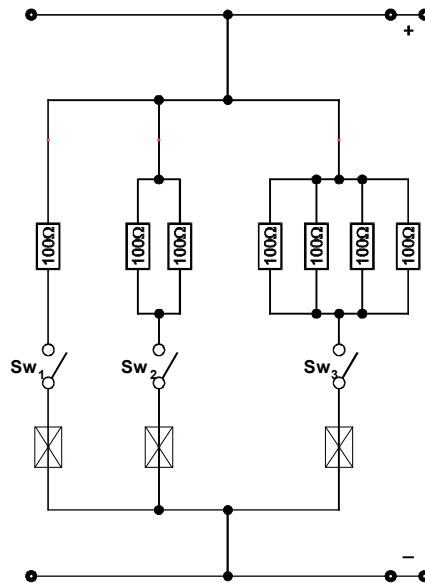


Fig. 8. Configuration of resistance load. Three switches ( $Sw_1$ ,  $Sw_2$ ,  $Sw_3$ ) allow to select 8 different values of resistance load. Notice the status of control LEDs of switched on load sections.

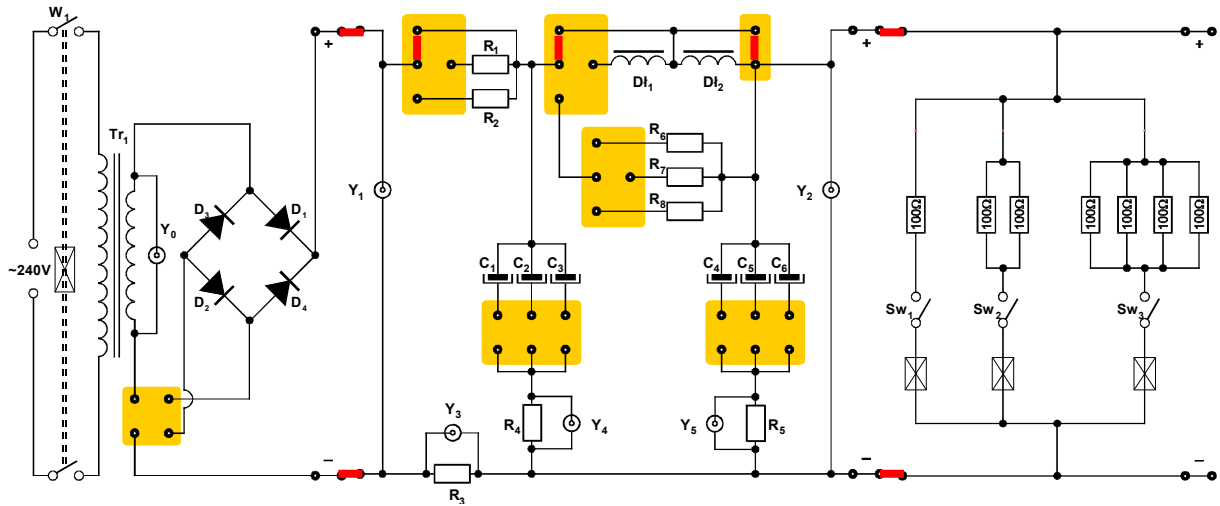


Fig. 9. Total schematic diagram of investigated setup to observe rectified voltage for the half or full-wave rectifier circuits.

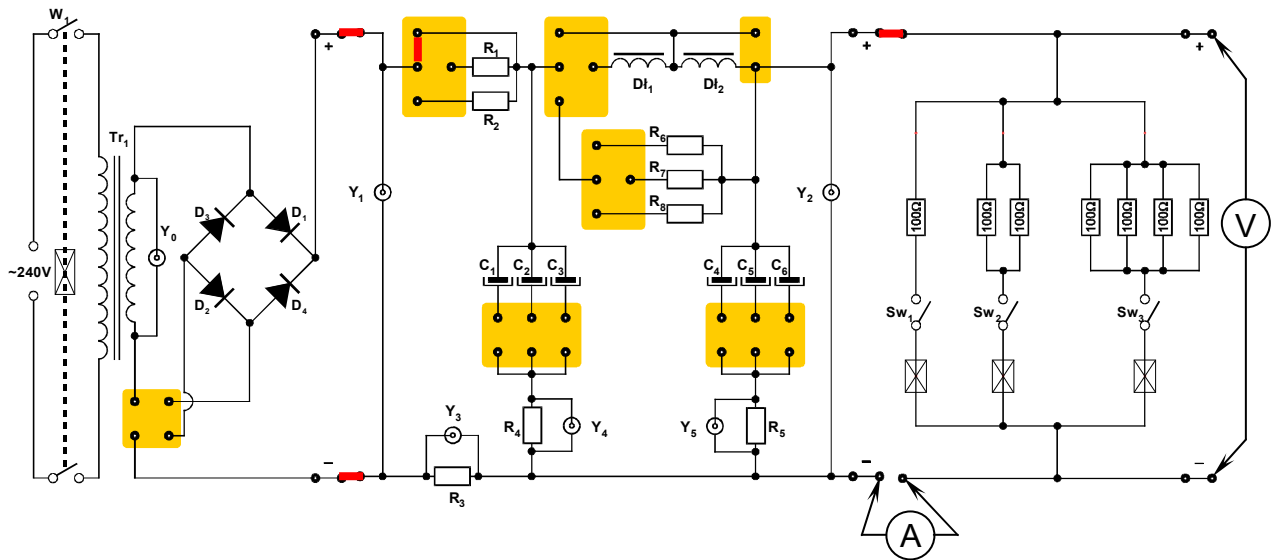


Fig. 10. Total schematic diagram of investigated setup to observe ripple voltage for different filters and various resistances of load.



## 5. Experimental procedure

### 5.1. Basic version

1. Connect the circuit according to the diagram presented in Fig. 9. Use the jumper to select the half-wave mode of rectifier (see Fig. 6a). Check if all of  $Sw_1$ ,  $Sw_2$ ,  $Sw_3$  switches are set to 0 ( $R_L \rightarrow \infty$ , minimum load). Connect the two channels of oscilloscope to  $Y_0$  and  $Y_1$  BNC connectors on the front panel of experimental module. Set the input amplification of the both oscilloscope channels to 5V/DIV. **NOTICE: the real gain of input channel connected to  $Y_0$  is 10V/DIV because of safety lab regulations (the voltage on  $Y_0$  is two times lower then the real output voltage of secondary winding of a transformer). Ask the supervisor to approve the circuit configuration before you switch on the power.** Use the  $W_1$  switch to power on the circuit. Draw oscillograms of input signal of supply voltage (before rectifier) and related output signal of rectified voltage – see Fig. 1.
2. Use the jumpers to select the full-wave mode of rectifier (see Fig. 6b). Draw the related oscillograms – see Fig. 2.
3. Repeat the measurements (described above in steps 1 and 2) for 3 different  $R_L$  loads. Use the  $Sw_1$ ,  $Sw_2$ ,  $Sw_3$  switches to select  $R_L$  values of load – minimum, maximum and third other. Draw related oscillograms.
4. Use the  $W_1$  switch to power off the circuit.
5. Connect the circuit according to the diagram presented in Fig. 10 to observe and measure the ripple voltage. Use the jumper to select the half-wave mode of rectifier (see the Fig. 6a). Check if all of  $Sw_1$ ,  $Sw_2$ ,  $Sw_3$  switches are set to 0 ( $R_L \rightarrow \infty$ , minimum load). Use the jumpers to select the simple capacitor filter at the middle front panel of module (see Fig. 7a). Set the capacitance to  $C = C_1$ . Select 200 or 400 V DC and 20A DC ranges of DMMs. **WARNING: you have to connect the red wire of DMM ammeter to terminal marked as 20A.** Connect the two channels of oscilloscope to  $Y_2$  and  $Y_3$  BNC connectors on the front panel of experimental module. Signal from  $Y_2$  allow to measure the ripple voltage of rectifier. **Ask the supervisor to approve the circuit configuration before you switch on the power.** Use the  $W_1$  switch to power on the circuit. Read the peak-to-peak ripple voltage  $U_{tpp}$  (see the Fig. 4) directly from the oscilloscope display. Notice the indications of DMMs ( $U_{wy}$ ,  $I_{wy}$ ). Write down the obtained results in the Table 1.
6. Make the measurements for minimum 3 different values of  $R_L$  load. Take into account the case of the minimum and maximum load ( $R_L \approx 14.3\Omega$ ). Write down the obtained results ( $I_{wy}$ ,  $U_{wy}$  and  $U_{tpp}$ ) in the Table 1.
7. Repeat the measurements (described above in steps 5 and 6) for step-by-step increased three different values  $C$  of capacitance filter and next for full-wave mode of rectifier. Write down the obtained results in the Table 1. (in the column “Rectifier mode” note down if the half or full-wave rectifier was investigated). Derive the  $C$  values of parallelly connected capacitances using data from “Table of passive electronic components” (see Appendix A1). Evaluate  $R_L$  loads using data from the front panel of experimental module.

Table 1. Simple capacitor filter.

Rectifier mode	#	C	$R_L$	$I_{wy}$	$U_{wy}$	$U_{tpp}$	$M_t$
		[ $\mu$ F]	[ $\Omega$ ]	[A]	[V]	[V]	

8. Repeat the measurements (described above in steps 5, 6, and 7) for LC filter of  $\Gamma$  type (see Fig. 7b). Write down the obtained results in the Table 2. (in the column “Rectifier mode” note down if the half or full-wave rectifier was investigated). Derive the values of C and L using data from “Table of passive electronic components” (see Appendix A1). Evaluate  $R_L$  loads using data from the front panel of experimental module.

Table 2. LC filter of  $\Gamma$  type.

Rectifier mode	#	C	L	$R_L$	$I_{wy}$	$U_{wy}$	$U_{tpp}$	$M_t$
		[ $\mu$ F]	[mH]	[ $\Omega$ ]	[A]	[V]	[V]	

9. Repeat the measurements (described above in steps 5, 6, and 7) for LC filter of  $\Pi$  type (see Fig. 7c). Write down the obtained results in the Table 3. (in the column “Rectifier mode” note down if the half or full-wave rectifier was investigated). Derive the values of C and L using data from “Table of passive electronic components” (see Appendix A1). Evaluate  $R_L$  loads using data from the front panel of experimental module.

Table 3. LC filter of  $\Pi$  type.

Rectifier mode	#	C	L	$R_L$	$I_{wy}$	$U_{wy}$	$U_{tpp}$	$M_t$
		[ $\mu$ F]	[mH]	[ $\Omega$ ]	[A]	[V]	[V]	

10. Use the  $W_1$  switch to power off the measuring setup.

## 5.2. Extended version

11. Repeat the measurements (described above in steps 5, 6, and 7) for RC filter of  $\Pi$  type (see Fig. 7d). Write down the obtained results in the Table 4. (in the column “Rectifier mode” note down if the half or full-wave rectifier was investigated). Derive the values of C and R using data from “Table of passive electronic components” (see Appendix A1). Evaluate  $R_L$  loads using data from the front panel of experimental module.

Table 4. RC filter of  $\Pi$  type.

Rectifier mode	#	C	R	$R_L$	$I_{wy}$	$U_{wy}$	$U_{tpp}$	$M_t$
		[ $\mu$ F]	[ $\Omega$ ]	[ $\Omega$ ]	[A]	[V]	[V]	

12. Use the  $W_1$  switch to power off the measuring setup.

## 6. Report elaboration

Report has to be composed of:

1. Front page (by using a pattern).
2. Description of experiment purposes.
3. Short introduction (basic definitions, formulas, description of used marks and symbols).
4. Schematic diagrams of tested circuits.
5. List of used instruments and devices (id number, type, setting and range values).
6. Measuring results (including oscillograms and tables).
7. Plots, calculations, analysis, interpretation and sub-conclusions related to all required points of “Experimental procedure”.
8. Remarks and final conclusions.

Use obtained results to evaluate the ripple factors  $M_t$  for all cases of measured filters (see Eq. 6). The values of  $M_t$  should be written down in the related data tables.

Moreover, calculate the theoretical values of the ripple factor  $M_t$  according to Eq. 8 for a full-wave rectifier with a simple capacitor filter (the case shown in Figs. 6b and 7a, and part of the results from Table 1). Compare these theoretical values with experimental ones.

Based on the obtained values of ripple factor choose the best two filters: the first one for maximum load of rectifier ( $R_L \approx 14.3\Omega$ ) and the second one for no load (minimum load) of rectifier ( $R_L \rightarrow \infty$ ). Notice “the best filter” means the voltage ripple is reduced so extremely as possible by the filter.

## 7. References

### 7.1. Basic reference materials

- [1] A. Rusek, *Podstawy elektroniki, część pierwsza*, WSiP, Warszawa, 1979.
- [2] K. Braclawski, A. Siennicki, *Elementy półprzewodnikowe*, WSiP, Warszawa, 1986.

### 7.2. Other reference materials

- [3] User manuals of the oscilloscope and DMMs:  
<http://fizyka.p.lodz.pl/pl/dla-studentow/fundamentals-of-electronics/>
- [4] <http://www.edw.com.pl/ea/>

## 8. Appendixes

### A1. Table of passive electronic components

$C_1=100\mu\text{F}$	$C_4=100\mu\text{F}$	$Dt_1=40\text{mH}$	$R_1=1\Omega$	$R_3=0,27\Omega$	$R_6=1\Omega$
$C_2=470\mu\text{F}$	$C_5=470\mu\text{F}$	$Dt_2=40\text{mH}$	$R_2=10\Omega$	$R_4=0,27\Omega$	$R_7=10\Omega$
$C_3=1000\mu\text{F}$	$C_6=1000\mu\text{F}$			$R_5=0,27\Omega$	$R_8=22\Omega$